

## Set C

### Question:

Write a sketch to display a message "iot is future " in lcd starting from the position 3<sup>rd</sup> column 1<sup>st</sup> row and simulate the same using tinker cad.

The image shows a student's handwritten work on a piece of lined paper. In the top right corner, there is a small box with 'Date' and 'Page' labels. The student has written their ID '20181CSE0621', name 'Sai Ram.K', and course 'G-CSE-10' on the left side. The date '29/04/2021' is written on the right. The assignment title 'IOT CA-3' is underlined in the center. Below it, 'Set-C' is also underlined. The student has provided three points: 1. Aim: To display the message "IoT is future" on LCD from 3rd column and first row. 2. Components: Arduino, Breadboard, jumper wires, potentiometer and LCD 16x2, Resistor. 3. Initial circuit design:-

Date \_\_\_\_\_  
Page \_\_\_\_\_

20181CSE0621  
Sai Ram.K  
G-CSE-10

IOT CA-3


Set-C

→ Aim: To display the message "IoT is future" on LCD from 3rd column and first row.

→ Components: Arduino, Breadboard, jumper wires, potentiometer and LCD 16x2, Resistor.

→ Initial circuit design:-

## Initial Circuit Design:

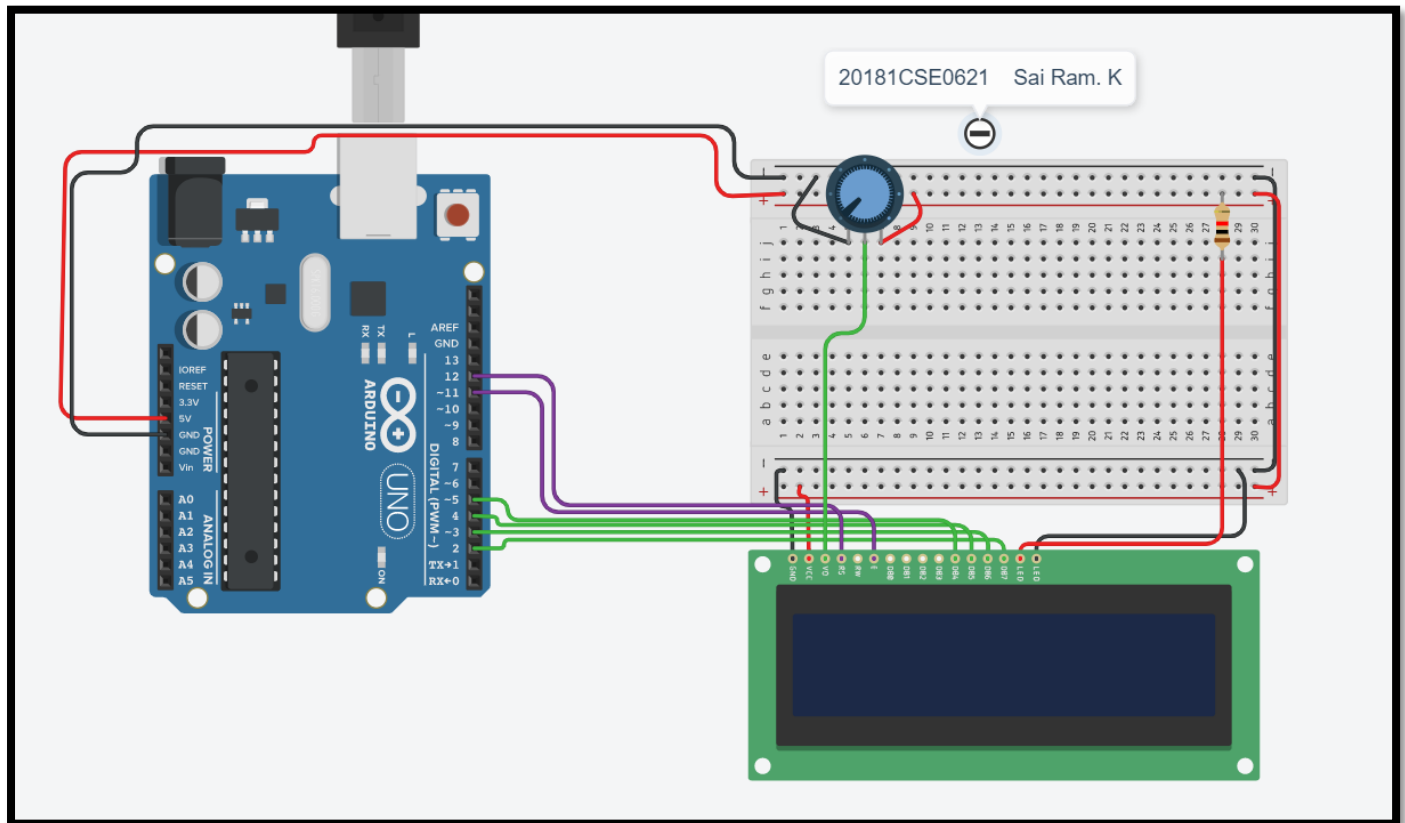

## Procedure:

Date \_\_\_\_\_  
Page \_\_\_\_\_

20181CSE0621

—> PROCEDURE:

Step 1: Assemble all the required components. Connect the +5V and Ground of arduino to the breadboard on either side for a common ground & 5V point using Jumper wires.

Step 2: Place the Potentiometer on the breadboard.

Step 3: Connect the Terminal-1 of potentiometer to ground & Terminal-2 to +5V (common point).

Step 4: Connect the Wiper of potentiometer to the Contrast pin of LCD 16x2.

Step 5: Connect pin 1 & pin 2 to ground & +5V respectively.

Step 6: Connect pin 4 i.e. Register Select to pin 12 of the arduino (can be connected to any digital pin).

Step 7: Connect pin 6 i.e. Enable pin to pin 11 of the arduino.

Step 8: Connect the DB pins from DB4 to DB7 to pins 2 to pin 5 of the arduino respectively.

Step 9: Connect pin 15 to a 1k $\Omega$  resistor and the other end of resistor to +5V.

Step 10: Connect pin 16 to ground.

Step 11: Switch on the circuit and we will find that the message "IoT is Future" will be displayed from the 3rd row and the 1st column of the LCD 16x2.

Sketch: